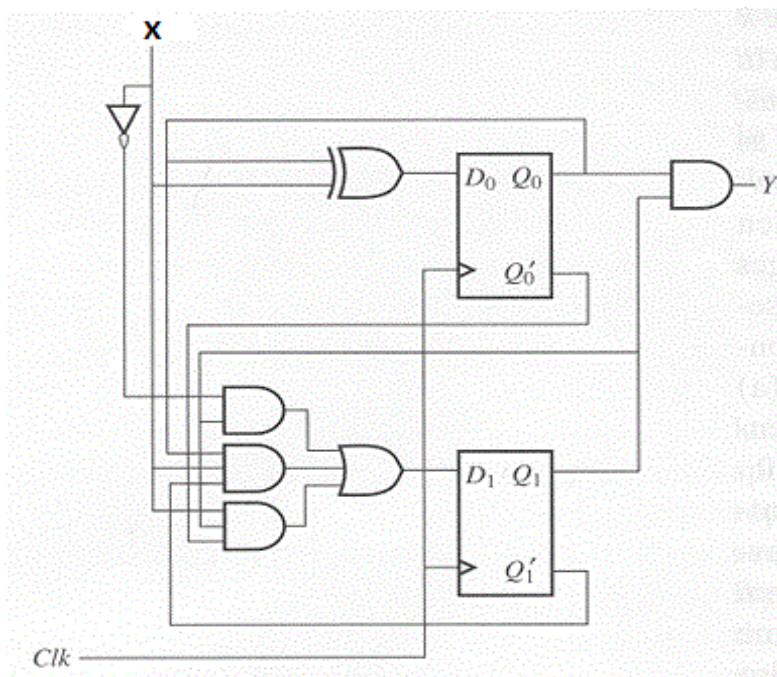


Course Code:	EE227
Semester:	Fall 2018
Total Marks:	40
Weight	15%
Page(s):	4
Roll No.	
Section:	

Question 1[10 Marks]: Consider given diagram



Present states		X (Input)	D ₀	D ₁	Next states		Y (Output)
Q ₀ (t)	Q ₁ (t)				Q ₀ (t+1)	Q ₁ (t+1)	
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

ii. Write next state equations [3]

Q_0 _____

Q_1 _____

Y _____

iii. Draw state diagram [2]

Question 2 [10 Marks]: Design a 4-bit mini-Process Unit that works according to the given functionality:

M_1	M_0	$F(A,B) = S_3S_2S_1S_0$	Function Description
0	0	$A - 2*B$	Subtract 2 times B from A
0	1	$A + 4*B$	Add 4 times B and A
1	0	$A + B$	Add A and B
1	1	$A + 1$	Increment A

Where A and B are two 4-bit numbers. M inputs to your mini-processor are control inputs. Partial design of the mini-processor is given below. **Your task is to add required logic in the design given below in order to make mini-processor fully functional.**

Note: Assume that you already have Decoder(s), Encoder(s), MUX(s), DMUX(s) and Multiplier(s) blocks available. **Properly label all blocks and inputs/outputs to get credit.**

Question 3: Implement the function given below

$$F(A,B,C,D) = \sum m(0,2,4,5,6,12,14)$$

- (a) [10 Marks] Using a 4x1 MUX and external Gates only. Take C and D as Selection Inputs and A and B as Data Inputs
- (b) [10 Marks] Using Decoder(s) and external NAND Gates only

Note: Properly label inputs and outputs to get credit

Input				Output
A	B	C	D	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

a)

b)